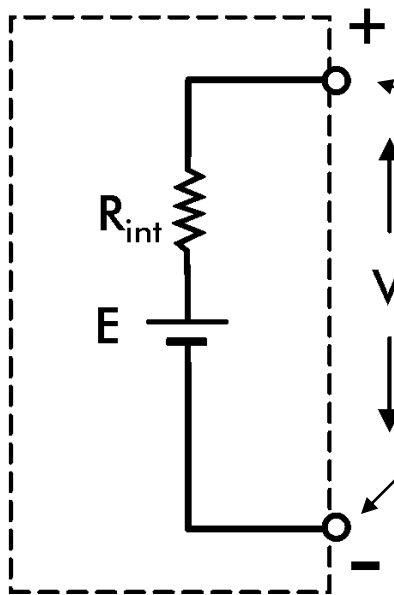

Internal Resistance and Resistivity in DC Circuits

AP Physics C

Internal Resistance

All components in a circuit off some type of resistance regardless of how large or small it is. Batteries especially have what is called an **internal resistance**, r .

DC power supply



Within the schematic it will be represented as a resistor symbol next to a battery symbol and between 2 points that represent the positive and negative terminals of the battery. Many times they are labeled with letters.

Since the battery is in effect a resistor, there is a voltage drop across it. Therefore there is only a certain amount of voltage that actually goes pout to the circuit. That voltage is called the **TERMINAL VOLTAGE**, V_T .

Internal Resistance

$\mathcal{E} = \text{EMF} = \text{maximum voltage}$

$V_T = V_{ab} = \text{terminal voltage}$


$$\mathcal{E} - Ir - V_{ab} = 0$$

$$V_{ab} = -rI + \mathcal{E}$$

Going around the circuit counterclockwise.

We define the **maximum voltage that the battery can produce the EMF.**

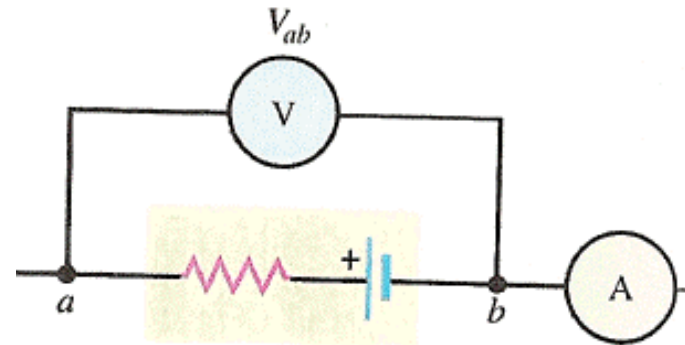
Some of the voltage will DROP across the battery. The rest will drop ACROSS the external circuit. **This is called the terminal voltage.**



To solve situations involving internal resistance we must use Kirchhoff's Voltage Law.

When KVL is re-arranged algebraically it looks like the slope of a line!

Internal Resistance is the SLOPE!

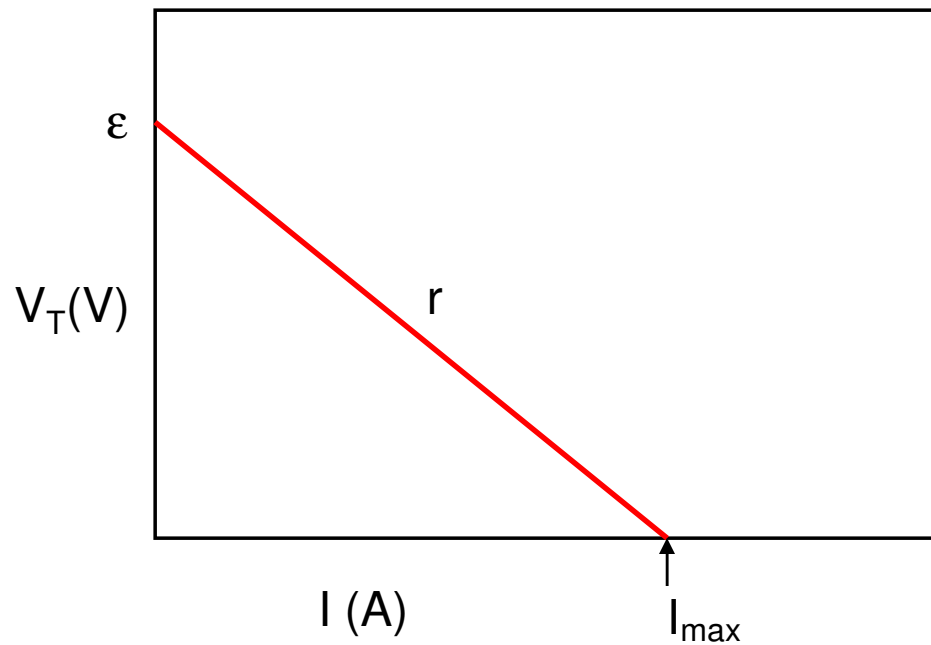

$$V_T = -rI + \epsilon$$

$$y = mx + b$$

There are many graphical applications as the equation above looks like the slope intercept form of a line. The terminal voltage is plotted on the Y-axis, the current is plotted on the X-axis, the internal resistance is the SLOPE, the EMF is the Y-intercept.

Example

Suppose we have a car battery with an emf = 13.8 V, under a resistive load of 20 Ω , the voltage sags to 11.8 V .

a) What is the battery's resistance?

$$V_T = IR_{Load}$$

$$11.8 = I(20)$$

$$I = 0.58 \text{ A} \leftarrow$$

The car's battery is in series with the load so the current is the SAME throughout the circuit.

$$V_T = -rI + \mathcal{E}$$

$$11.8 = -r(?) + 13.8$$

$$r = 3.45 \Omega$$


b) What is the rate at which energy is dissipated in the battery?

$$P = VI$$

$$P = (2)(0.58) = 1.16 \text{ W}$$

Resistivity

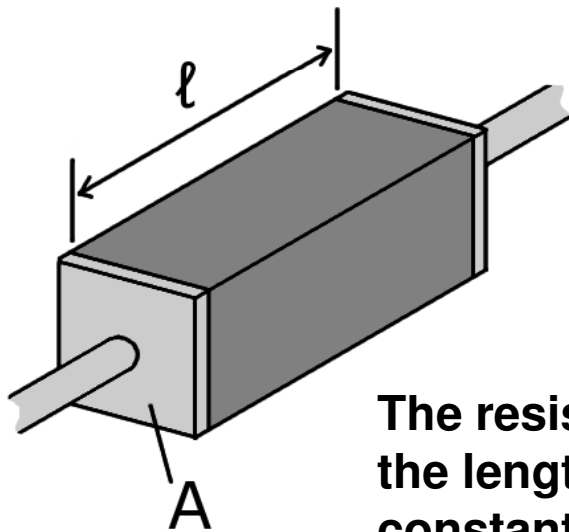All wires in a circuit also contribute to the overall resistance in a circuit. Even though the value is often small and negligible, it is often important to determine the value for the resistance of a wire if it is thick or long. This being said, the resistance is dependant on the geometry of the material



$$R \propto l \quad R \propto \frac{1}{A}$$

ρ = Resistivity Constant

$$R = \frac{\rho l}{A}$$

The resistance of the wire is **DIRECTLY** proportional to the length and inversely proportional to the area. The constant of proportionality is then defined as the **RESISTIVITY**, which is based on material type.

Example

Calculate the resistance of a one meter length of 24 SWG Nichrome wire.

SWG = Standard Wire Gauge

24 *SWG* = 0.558mm in diameter

$$\rho_{\text{Nichrome}} = 1.10 \times 10^{-6} \Omega m$$

$$R = \frac{\rho l}{A} = \frac{(1.10 \times 10^{-6})(1)}{\pi(2.795 \times 10^{-4})^2} = \mathbf{4.48 \Omega}$$

As you can see, using significant amounts of wire can greatly influence the voltage drops, current, and power produced in circuits.
